

Digital Logic and Computer Organization

Combinational Logic - Analysis and Design

Combinational Circuit

- A circuit consists of an inter-connection of logic gates.
- A logic circuit is combinational if its output(s) are a function of only the present inputs at any time.
- The inputs to a circuit can be viewed as binary variables from an external source.
- The outputs of a circuit are variables produced by the circuit based on the input signals and go to external destinations.
- For n input variables, there are 2^n possible combination of the binary inputs.
- For each distinct input combination, there is one value for each output variable.

Analysis of Combinational Circuits

- How to make sure the circuit to be analyzed is combinational? - In the schematic, there is no feedback paths or memory elements.
- Analyze by establishing a truth table: for each input combination, trace the schematic to establish its output.
- Literal analysis
 - Use meaningful symbols to name the output of each gate in the circuit;
 - Starting from the gates whose inputs are circuit inputs, find the Boolean functions for these gates;
 - For those gates whose inputs include the output of other gates whose functions are already established, find the Boolean functions for these gates;
 - Repeat the previous step until the Boolean function of the circuit's output is found.

Design Procedure

- From the specifications of the circuit, determine the required number of inputs and outputs and assign a symbol to each; (determine the interface of the circuit;)
- Derive the truth table that defines the required relationship between inputs and outputs; (determine the behaviour of the circuit;)
- Obtain the simplified Boolean function for each output as a function of the input variables; (determine the functionality of the circuit;)
- Draw the logic schematic; (determine the structure of the circuit;)
- Verify the correctness of the design by building a prototype or by simulation.

Design Examples/ Applications

- Half Adders



Half Adder

Augend Input A	Addend B	sum output S	carry C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = \bar{A}B + A\bar{B}$$

$$= A \oplus B$$

$$C = A \cdot B$$

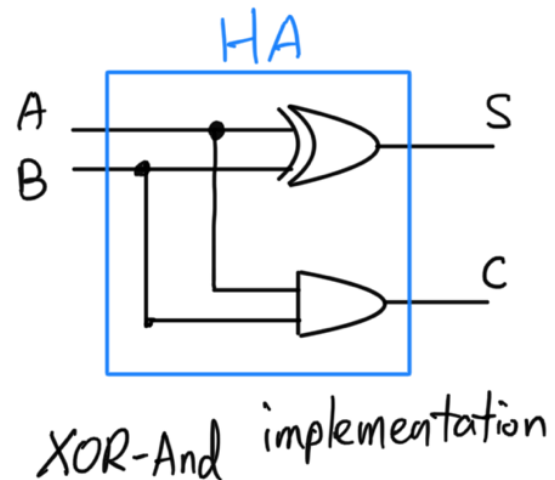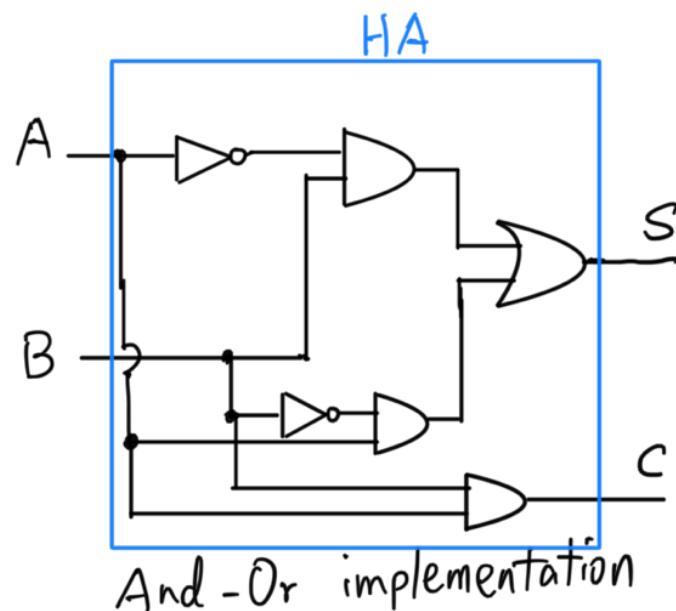

Full Adder


- Full Adder: Sum-of-Product; 2 Half Adders and an OR

Full Adder

Input			Output	
A_i	B_i	C_i	S_i	C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S_i = \bar{A}_i \bar{B}_i C_i + \bar{A}_i B_i \bar{C}_i + A_i \bar{B}_i \bar{C}_i + A_i B_i C_i$$

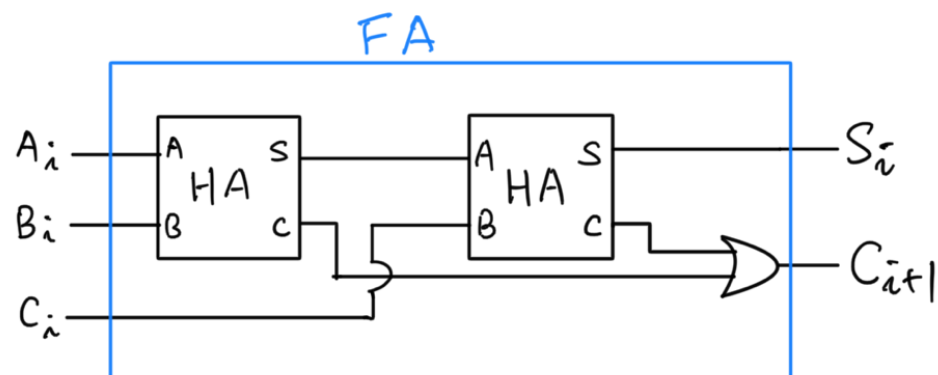
$$C_{i+1} = A_i B_i + A_i C_i + B_i C_i$$



Binary Adder


- Binary Adder: Multi-bit ripple carry Adder

4-bit Binary Adder

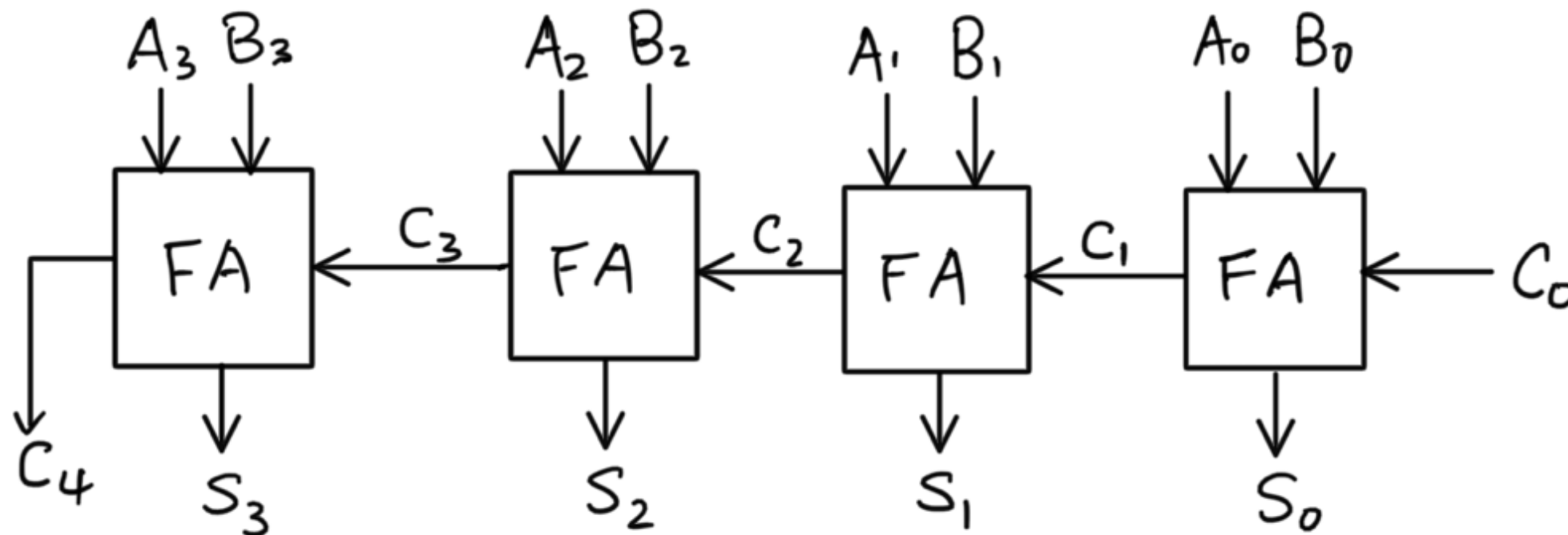

Binary Adder

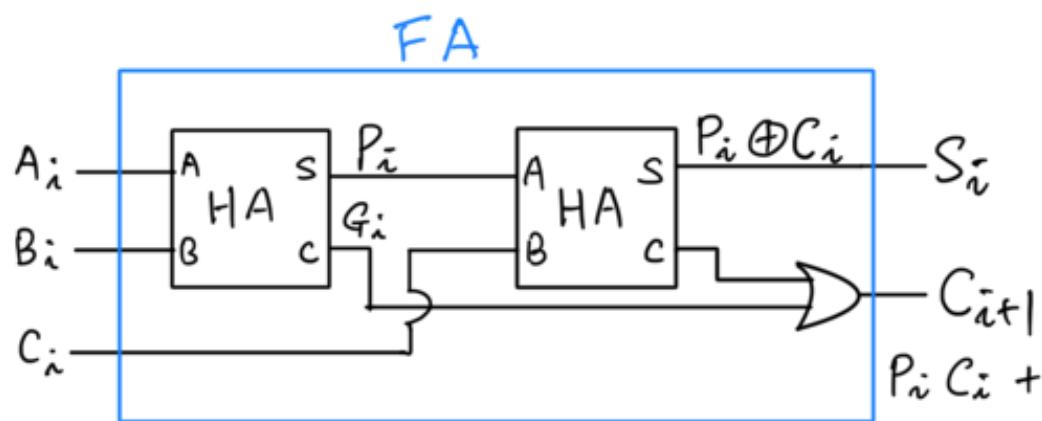- Issue: Carry propagation causing delays
- Solution: Carry lookahead



Carry Propagate $P_i = A_i \oplus B_i$
 Carry Generate $G_i = A_i B_i$



$C_0 = \text{input Carry}$

$$C_1 = G_0 + P_0 C_0$$


$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 (G_0 + P_0 C_0) \\ = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

Binary Adder with Lookahead

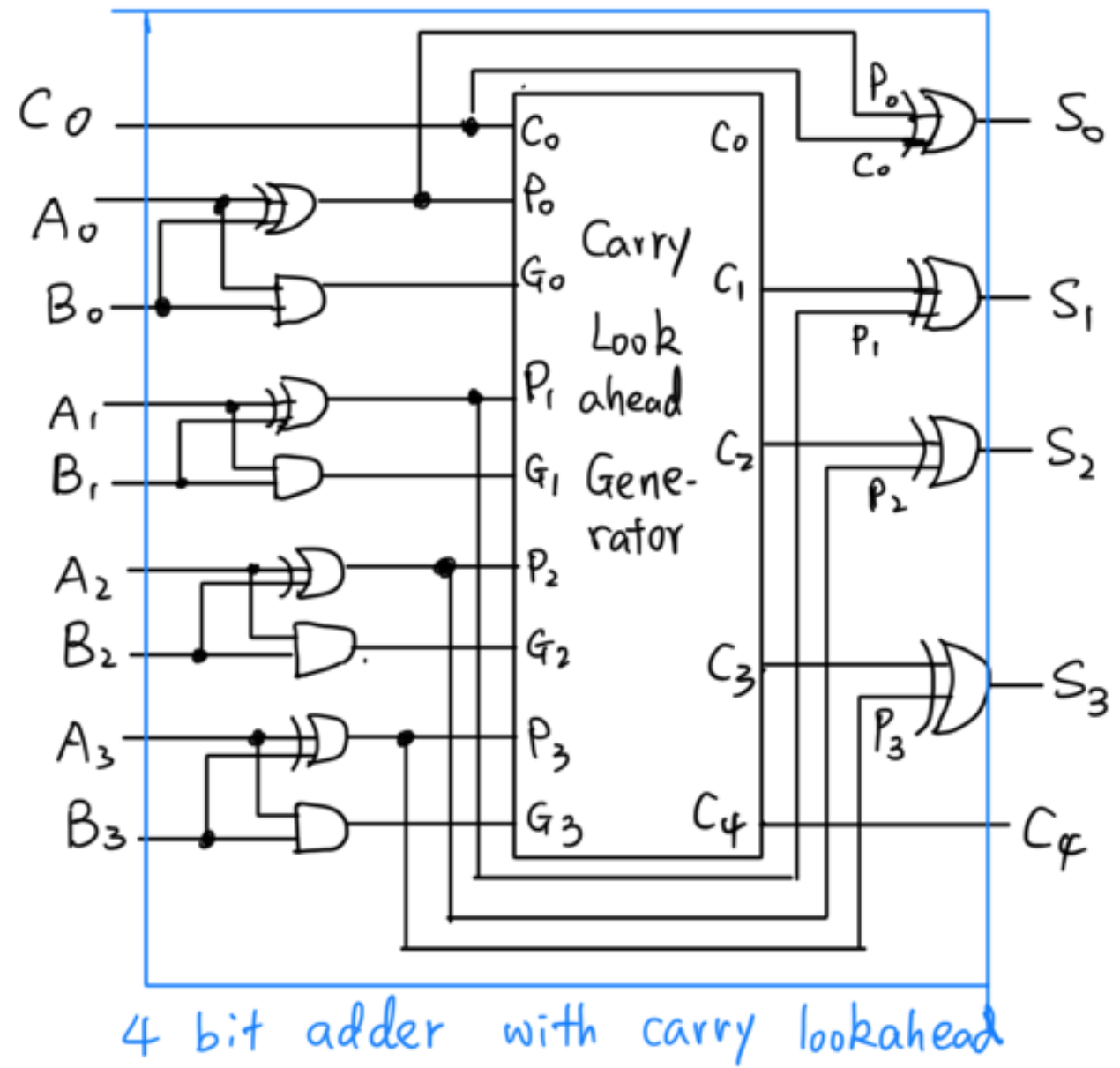 

Binary Subtractor

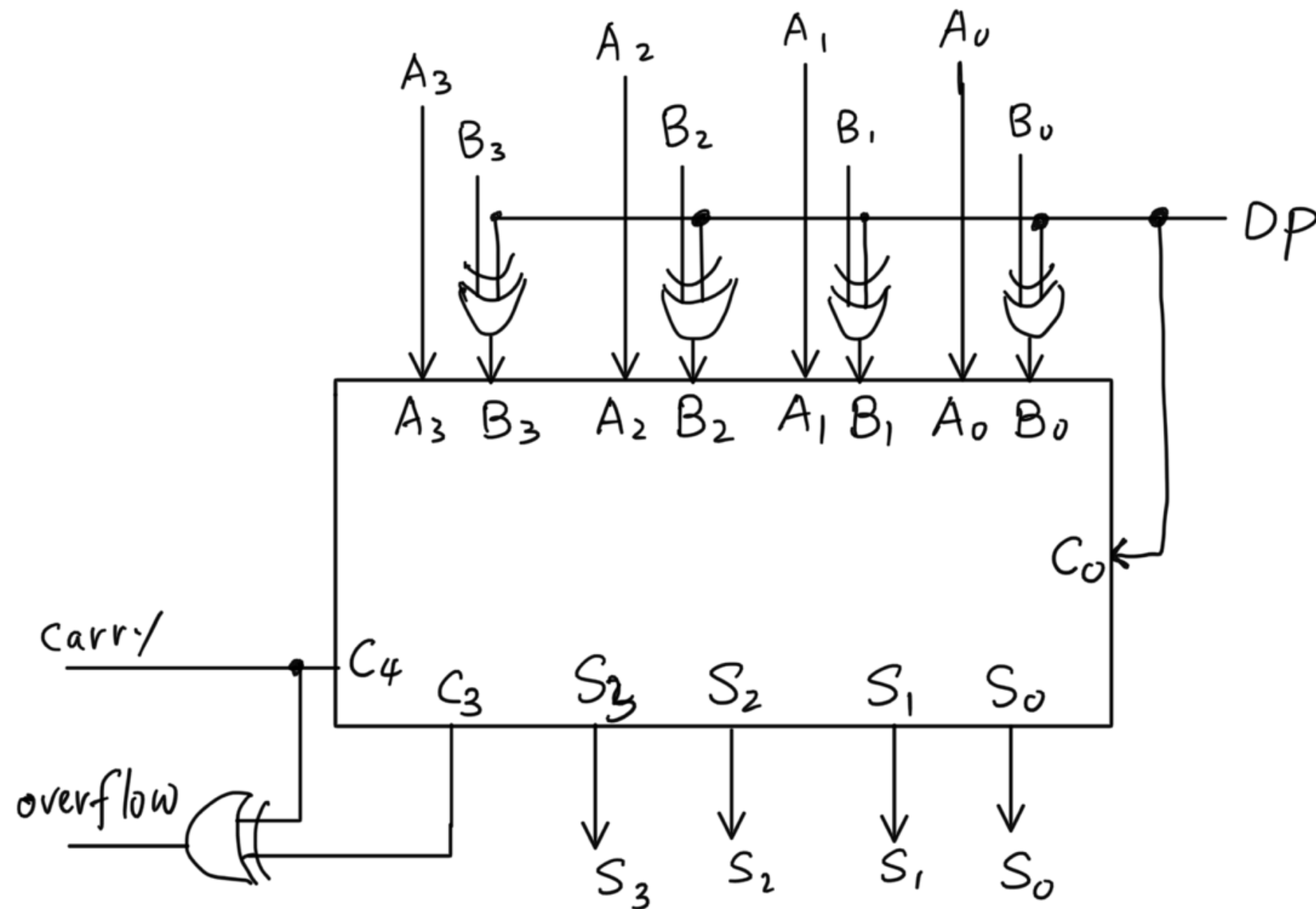


Magnitude Comparator

$$X_i = A_i B_i + \bar{A}_i \bar{B}_i \quad \text{for } i=0,1,2,3$$


$$F_{A=B} = X_3 \cdot X_2 \cdot X_1 \cdot X_0$$

$$F_{(A>B)} = A_3 \bar{B}_3 + X_3 A_2 \bar{B}_2 + X_3 X_2 A_1 \bar{B}_1 + X_3 X_2 X_1 A_0 \bar{B}_0$$

 
$$F_{(A<B)} = \bar{A}_3 B_3 + X_3 \bar{A}_2 B_2 + X_3 X_2 \bar{A}_1 B_1 + X_3 X_2 X_1 \bar{A}_0 B_0$$



Decoder

 


2-to-4 decoder

 

2-to-4 decoder
with active-low enable
(0 means selected)

E	X	Y	D_0	D_1	D_2	D_3
1	x	x	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

 


3-to-8
decoder
with enable

Encoder & Priority Encoder


Input				output	
D_0	D_1	D_2	D_3	X	Y
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

$X = D_2 + D_3$
 $Y = D_1 + D_3$

Input				output		
D_0	D_1	D_2	D_3	X	Y	Valid
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	1	1	1	1	1

 


Multiplexer

 

Implement Function using Multiplexer

Input			output
X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$F = 0$
 $F = \bar{Z}$
 $F = Z$
 $F = 1$

 

Binary Multiplier

$$\begin{array}{r}
 B_3 B_1 \\
 \times A_1 \\
 \hline
 A_0 B_3 B_2 B_1 B_0 \\
 + A_1 B_3 B_2 B_1 B_0 \\
 \hline
 P_5 P_4 P_3 P_2 P_1 P_0
 \end{array}$$

