


Digital Logic and Computer Organization

Sequential Logic — Gated Latches



Asynchronous Problems

- Latches are asynchronous memory elements;
- Latch outputs are updated whenever its inputs change according to the appropriate characteristic equation;
- Problem: erratic state changes (think about the JK latch when $JK = 11$, or T latch when $T = 1$);
- How to fix it?
 - impose a synchronous timing discipline
 - add an enable (clock) signal as a gate keeper


Gated SR Latch

 

Gated D Latch

  

Gated JK Latch

 

Gated T Latch

