


Digital Logic and Computer Organization

Sequential Logic — Flip Flops

Problems with Gated Latches

- Gated latches are still not well suited for synchronous sequential systems because the potential of multiple state changes in one clock cycle.
- How to fix it?
 - use a master-slave configuration
 - shorten clock pulse so that there is only one state change per clock cycle (not likely)
 - use edge triggered flip flops


Negative Master-Slave SR Flip Flops

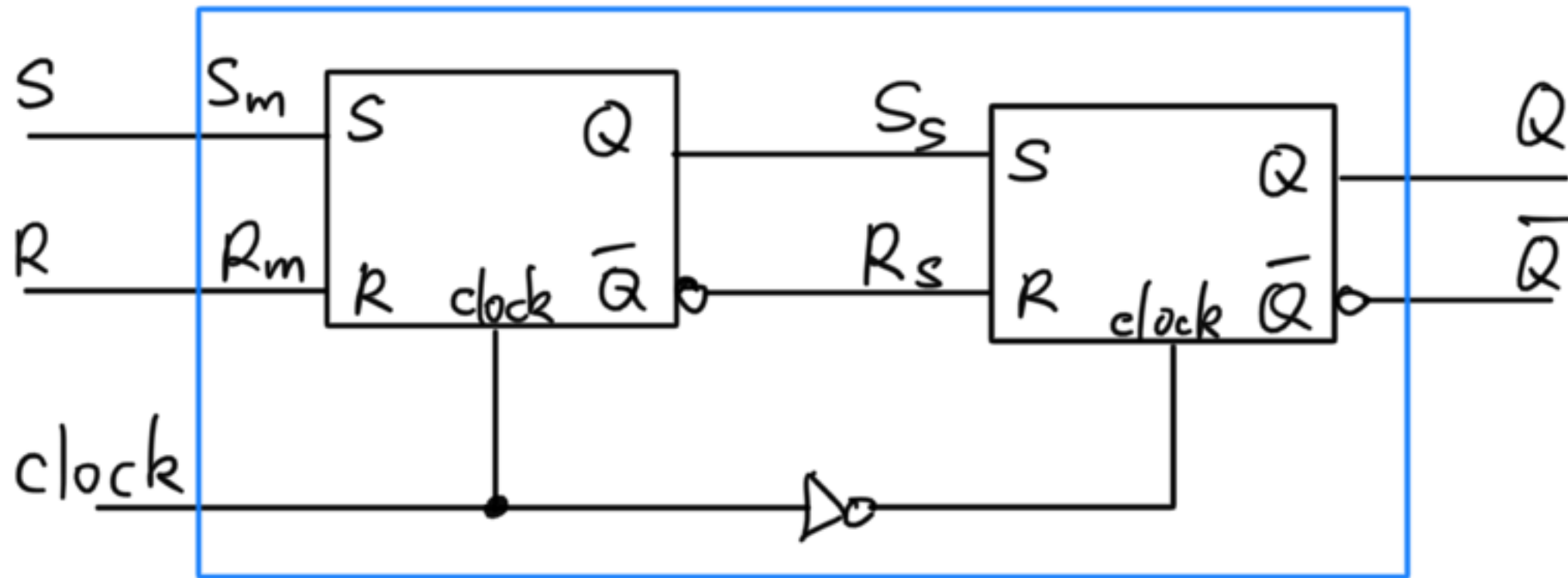

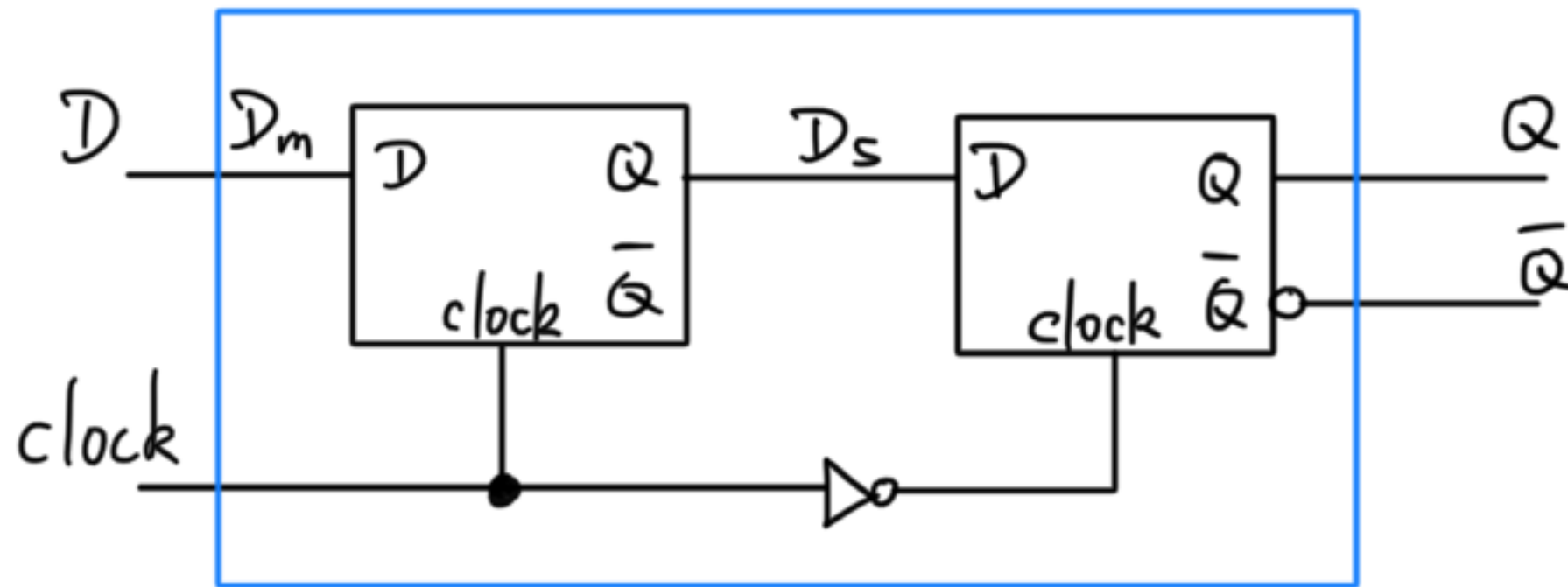
Problem

- The previous device is pulse triggered
- When the master is enabled, a glitch can incorrectly set/reset the master output, which is also the slave input
- Fix: move to edge-triggered devices
 - Positive edge triggered: outputs are generated on the rising edge
 - Negative edge triggered: outputs are generated on the falling edge



Negative Edge Triggered Master-Slave Realization D Flip Flop



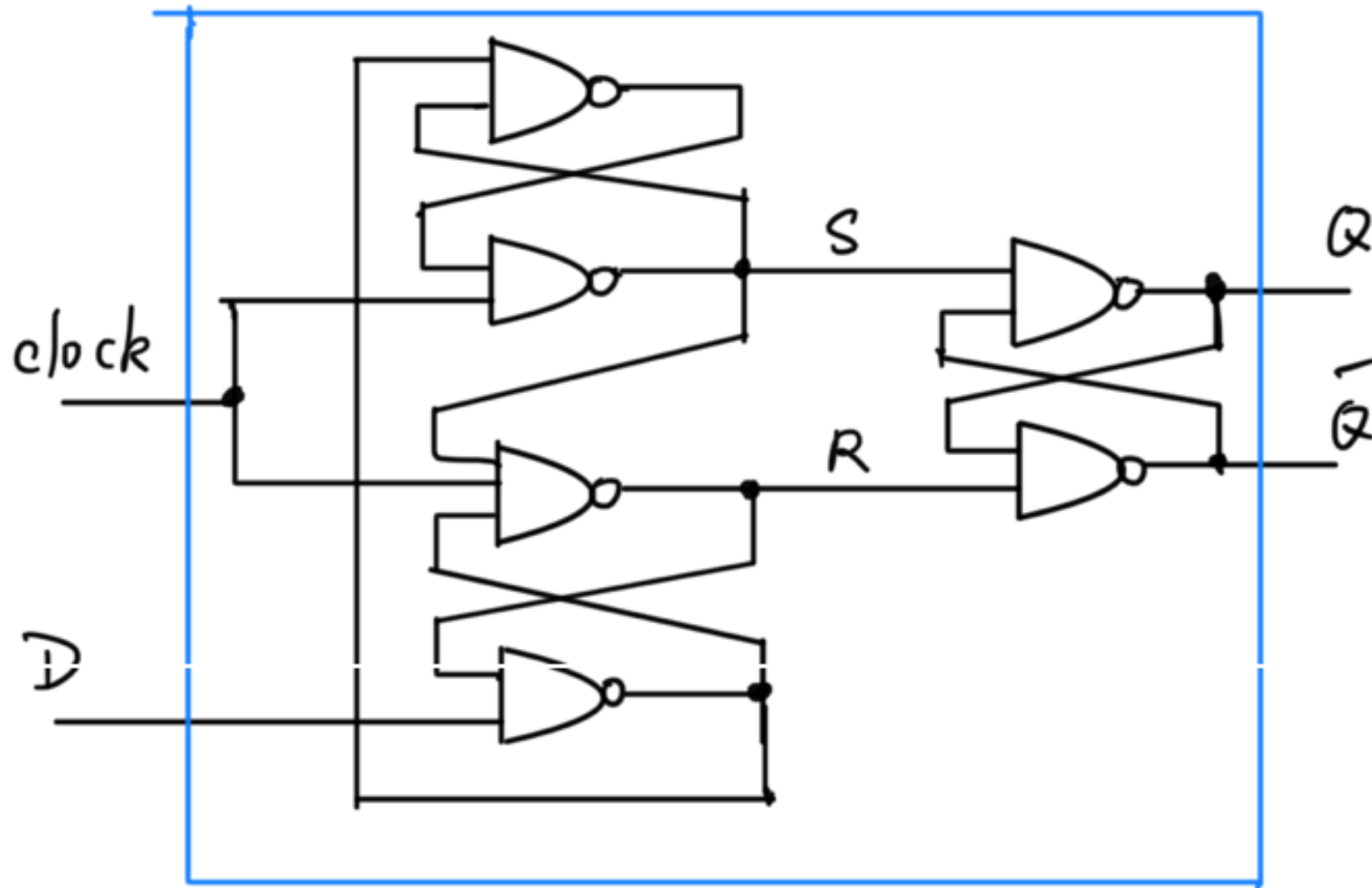Positive Edge Triggered Alternative Realization D Flip Flop




Edge Triggered D Flip Flop Symbols

 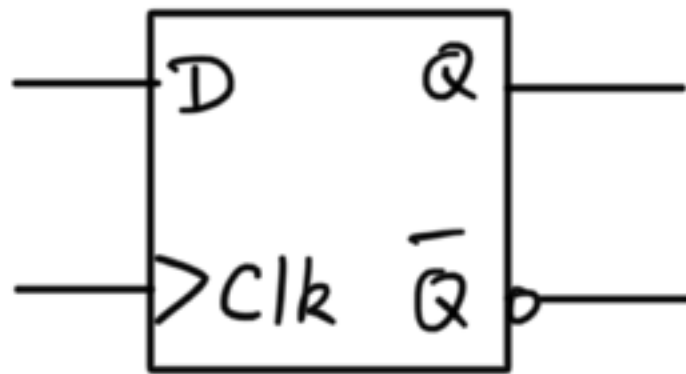

Excitation Table

Q	Q ⁺	D
0	0	0
0	1	1
1	0	0
1	1	1


Edge Triggered SR Flip Flop

 

Excitation Table

Q	Q ⁺	S	R
0	0	0	x
0	1	1	0
1	0	0	1
1	1	x	0


Edge Triggered JK Flip Flop

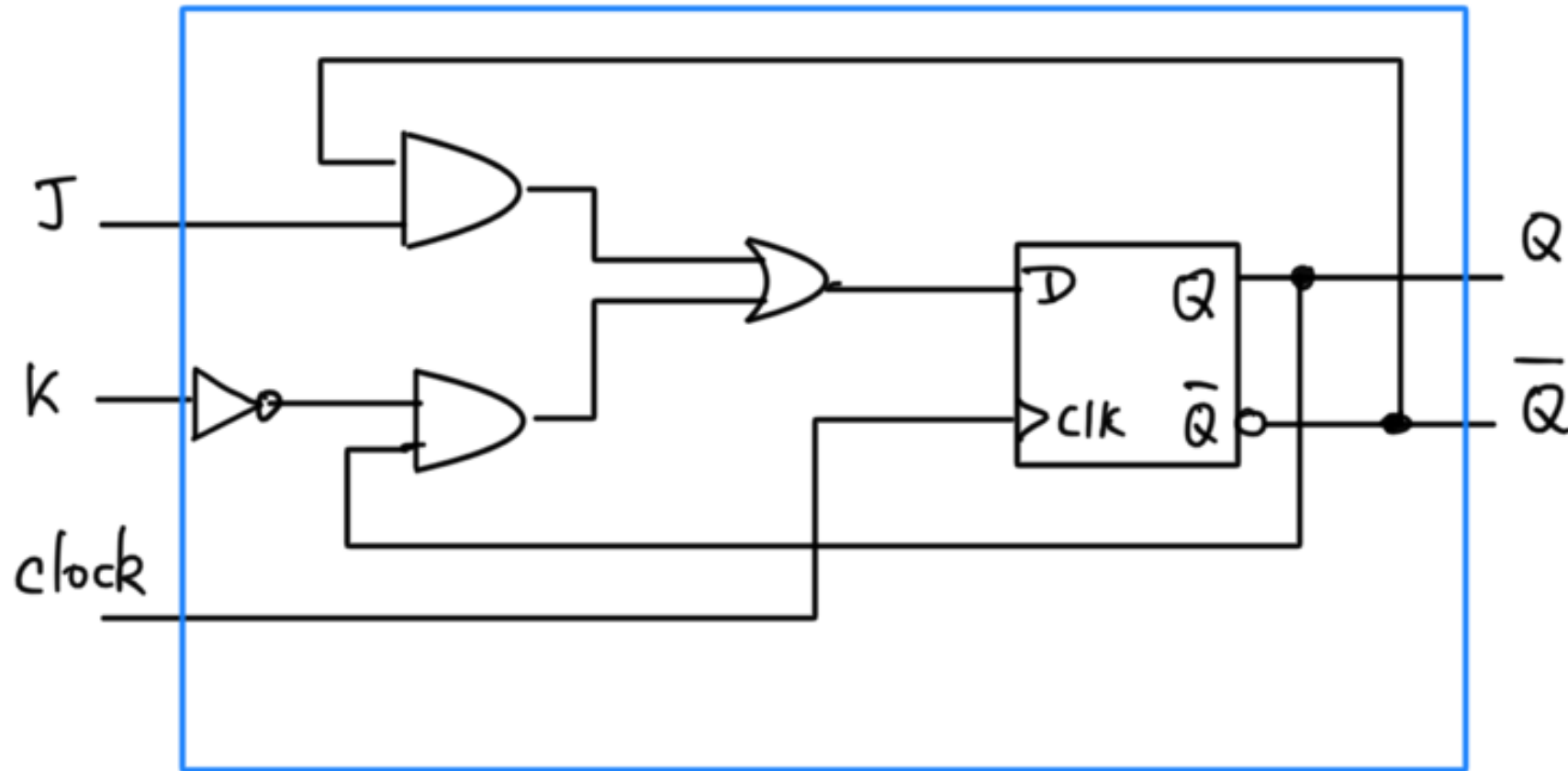

Excitation Table

Q	Q^+	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0



Edge Triggered T Flip Flop

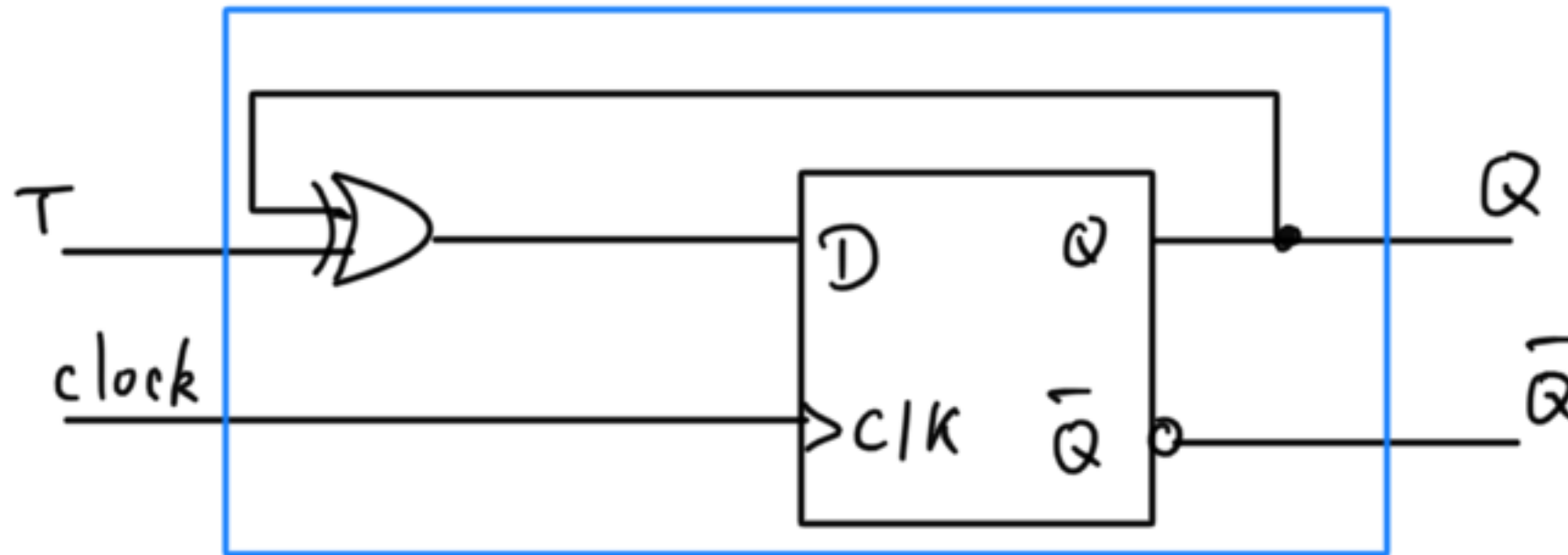

Excitation Table

Q	Q ^f	T
0	0	0
0	1	1
1	0	1
1	1	0

 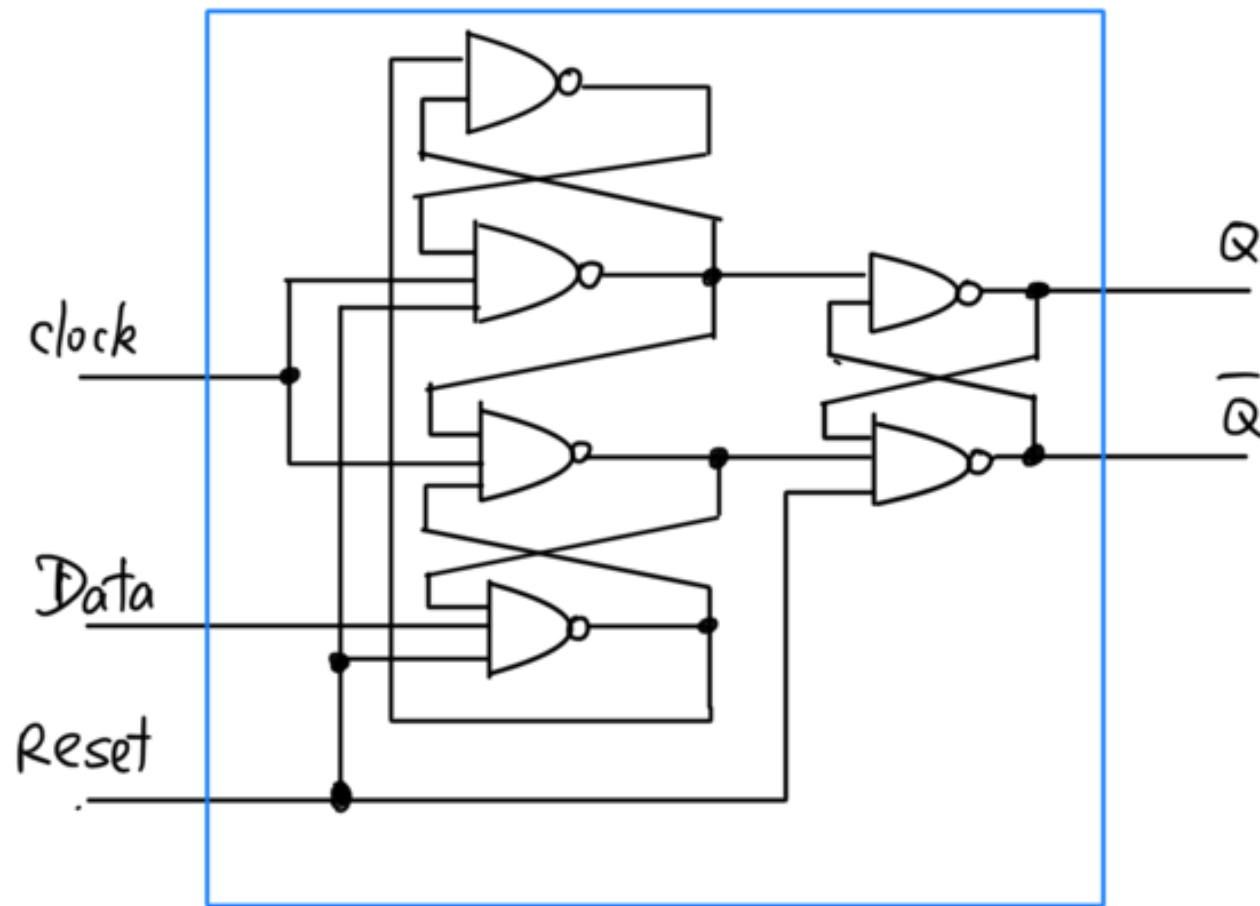Edge Triggered D Flip Flop with Asynchronous Reset



Reset	Clock	Data	Q	\bar{Q}
0	x	x	0	1
1	↑	0	0	1
1	↑	1	1	0