#### **Computer Science CSCI 355**

#### **Digital Logic and Computer Organization**

Dr. Peter Walsh Department of Computer Science Vancouver Island University peter.walsh@viu.ca

1: Computer Science CSCI 355 — Lecture 17

## Synchronous Sequential Systems

Latches are not well suited for synchronous sequential systems because they operate in an asynchronous fashion.

 $\bigcirc$  Inputs Change


- latch outputs are updated according
  - to the appropriate characteristic equation


○ Result


• erratic state changes


⊃ Fix

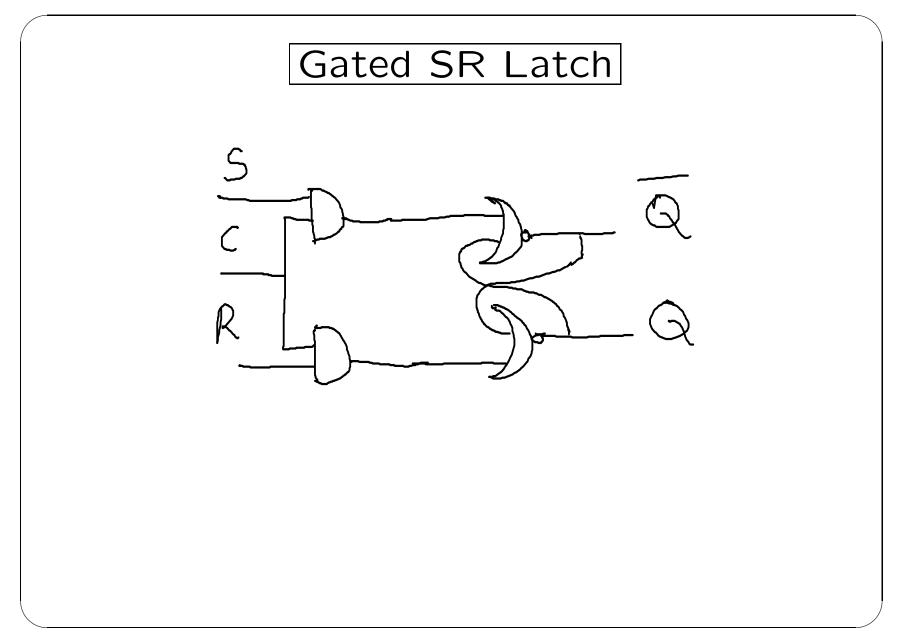
- impose a synchronous timing discipline
- add an enable (clock)



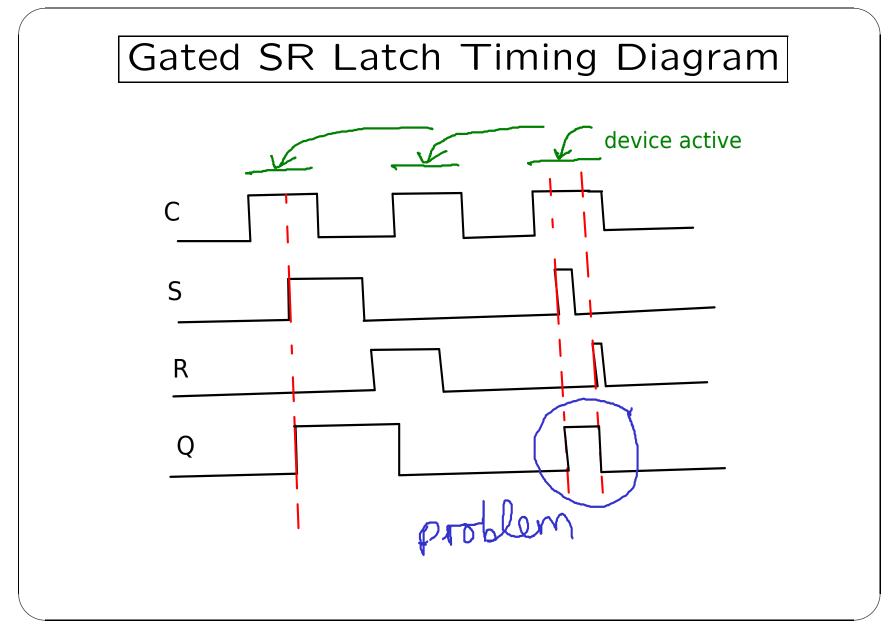

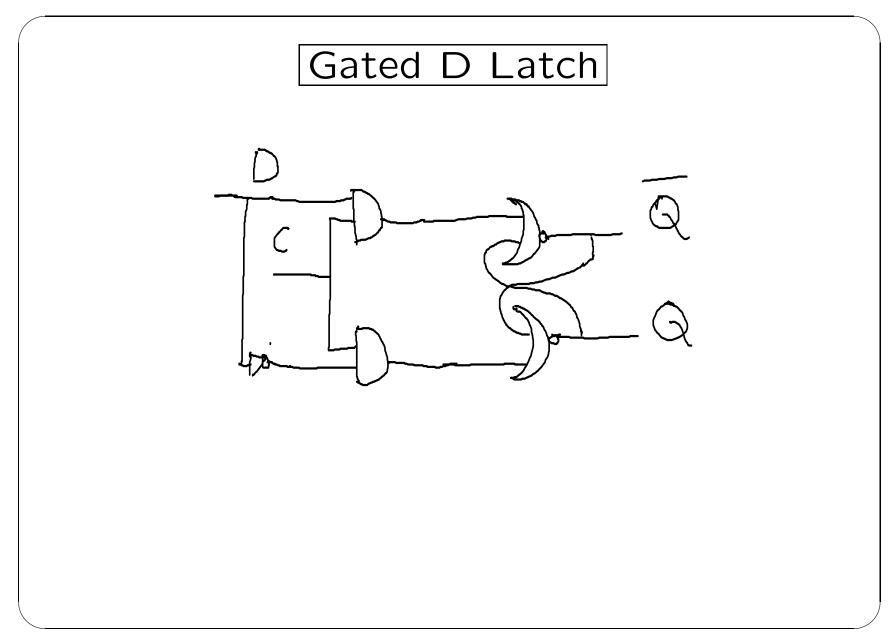


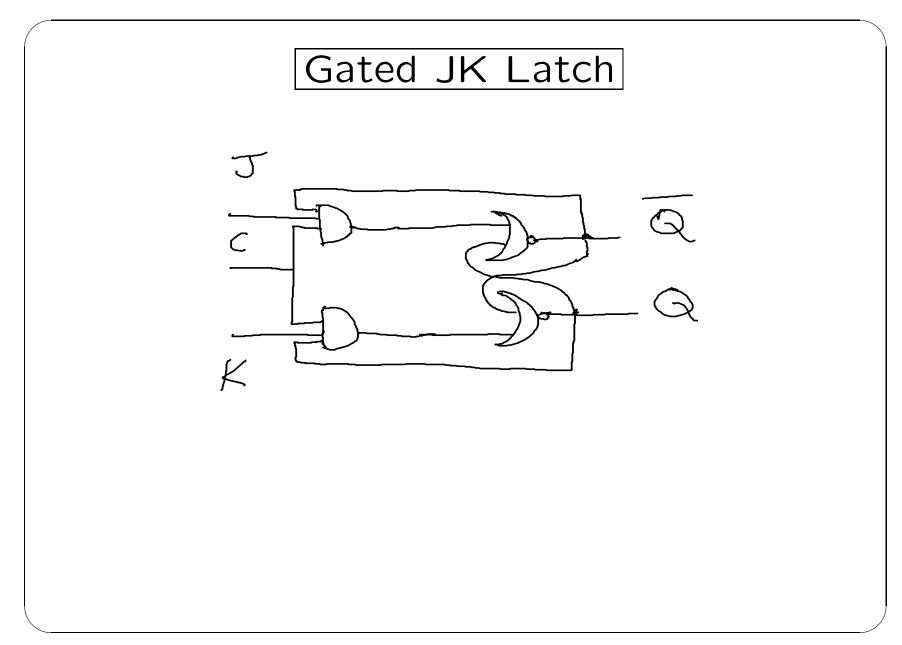

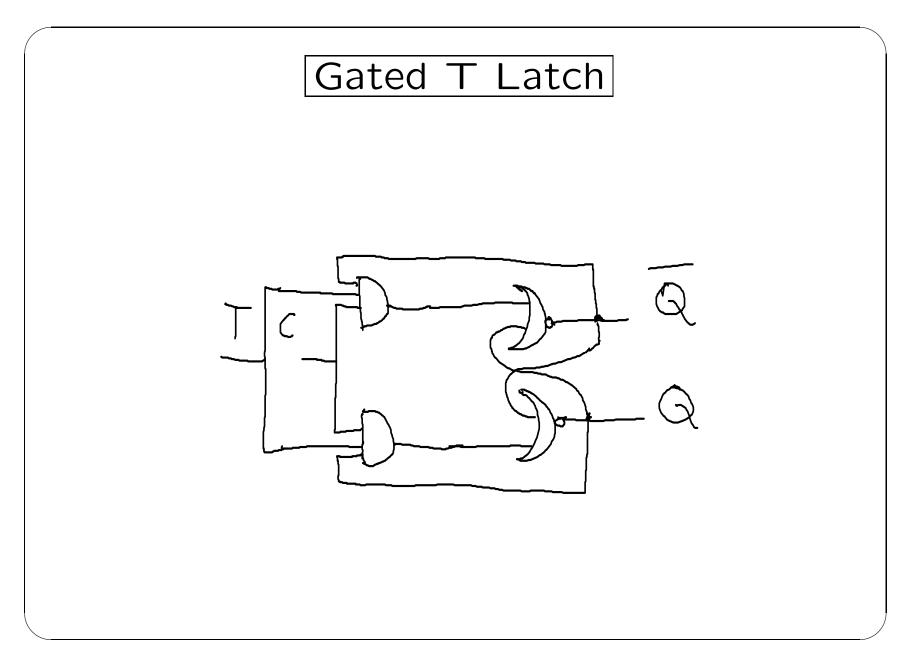
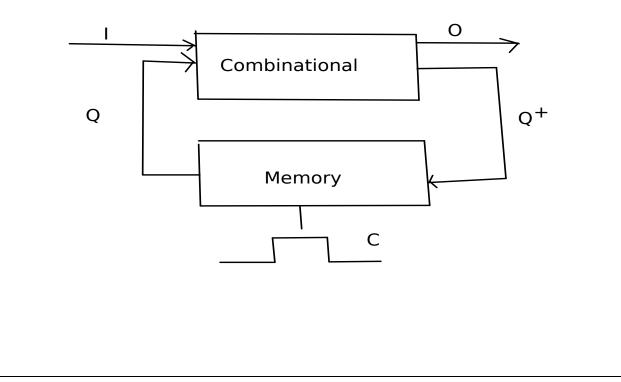
# Synchronous Sequential Systems

Gated Latches are not well suited for synchronous sequential systems because of the potential of multiple state changes per clock cycle.



### Synchronous Sequential Systems cont.

 $\bigcirc$  Inputs Change (during a clock cycle)

• gated latch outputs are updated according to the appropriate characteristic equation

🔿 Result

• possible multiple state changes

⊖ Fix

- shorten clock pulse such that memory contents are only updated once per clock cycle
- use a master-slave configuration

# Master-Slave Flip Flops (FF)

○ Pulse Triggered


 both the rising edge and the falling edge of the clock pulse are used to sample inputs and generate outputs

○ Positive Pulse Triggered


- inputs are sampled on the falling edge
- outputs are generated on the rising edge


○ Negative Pulse Triggered

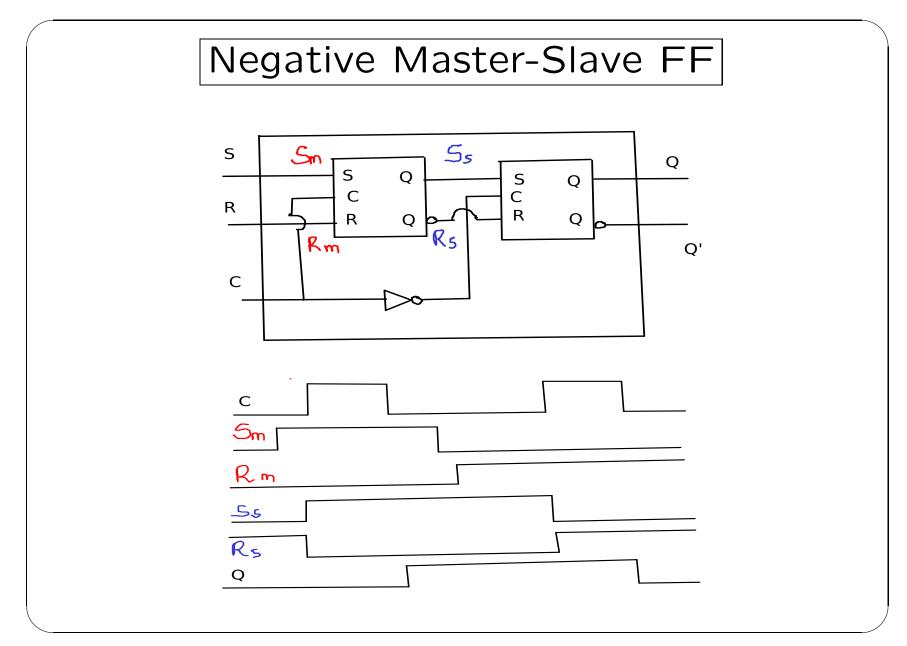- inputs are sampled on the rising edge
- outputs are generated on the falling edge



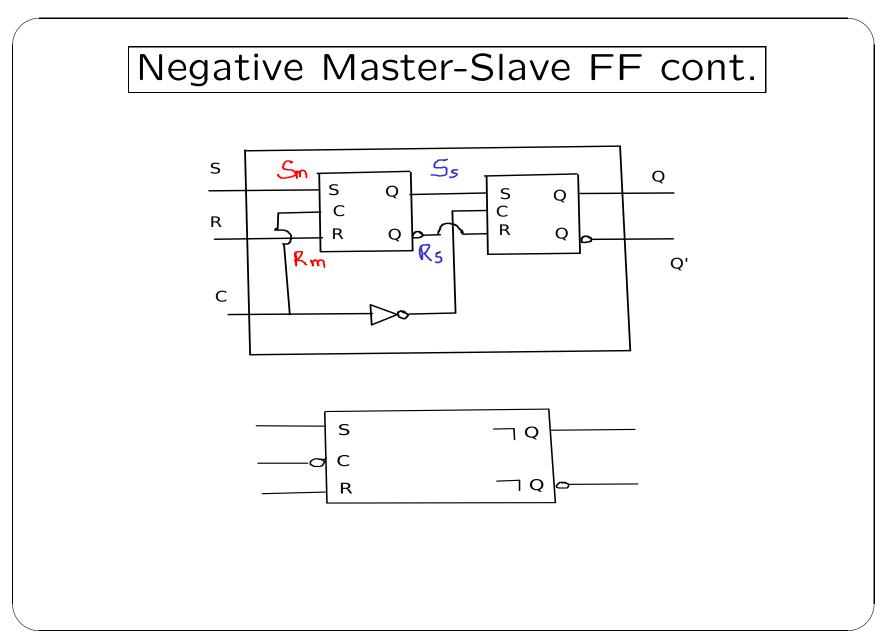11: Computer Science CSCI 355 — Lecture 17



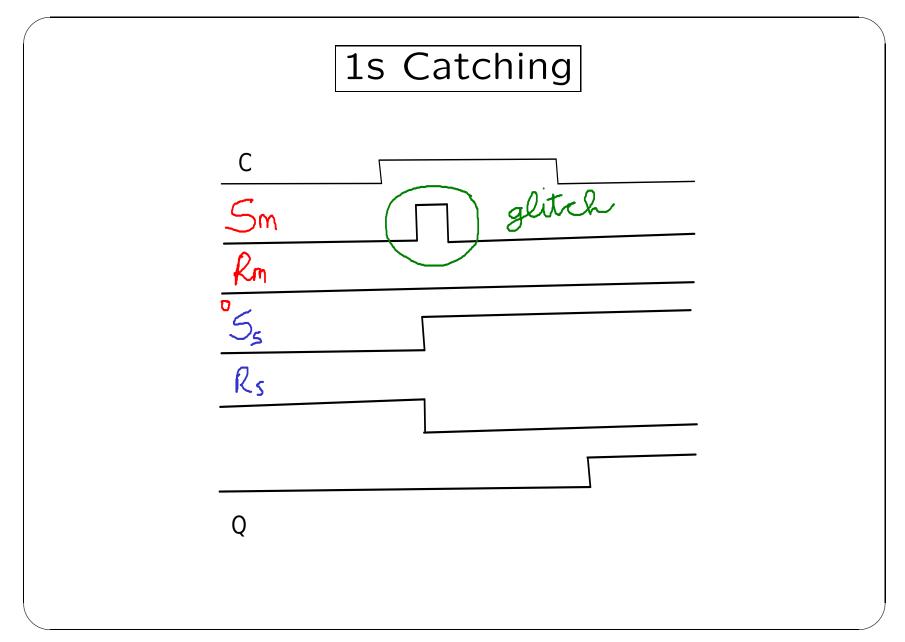

## Synchronous Sequential Systems

Master Slave FFs are not well suited for synchronous sequential systems because of "wrong" single state change.

○ Problem

 when the master is enabled, a glitch can incorrectly set/reset the master output (slave input)

⊖ Fix

- remove hazards
- move to edge-triggered devices