

Computer Science CSCI 355

Digital Logic and Computer Organization

Dr. Peter Walsh


Department of Computer Science

Vancouver Island University

peter.walsh@viu.ca


Counters

LD	CE	SCLR	L[2:0]	Operation	Priority
1	-	-	value	load value LD	0
0	1	0	-	count up CNT	1
0	0	1	-	clear CLR	2
0	0	0	-	nop NOP	3

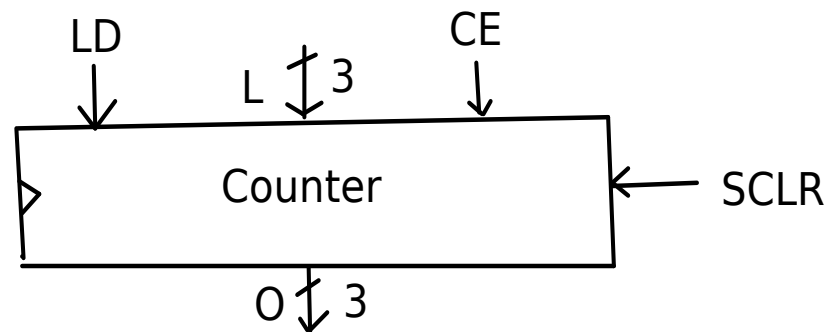


FSMs Using Counters

- use the counter to store state

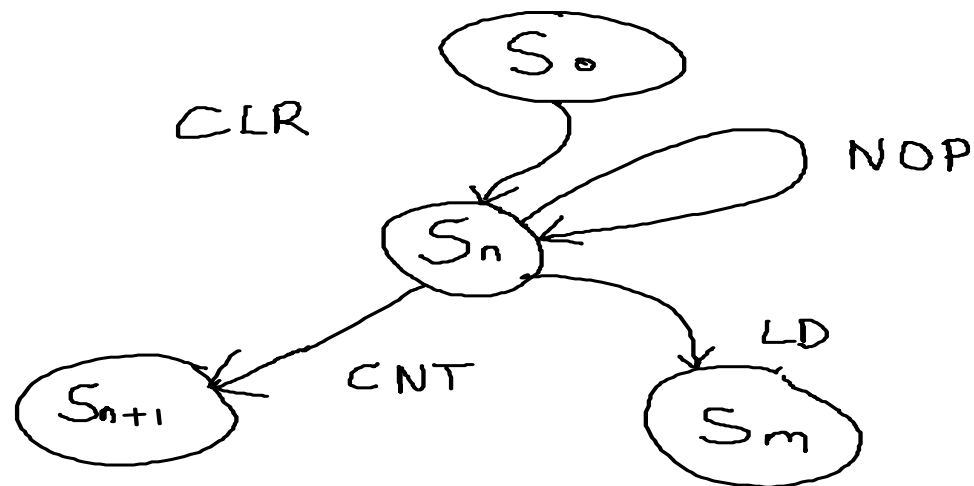


SSBC Control Unit

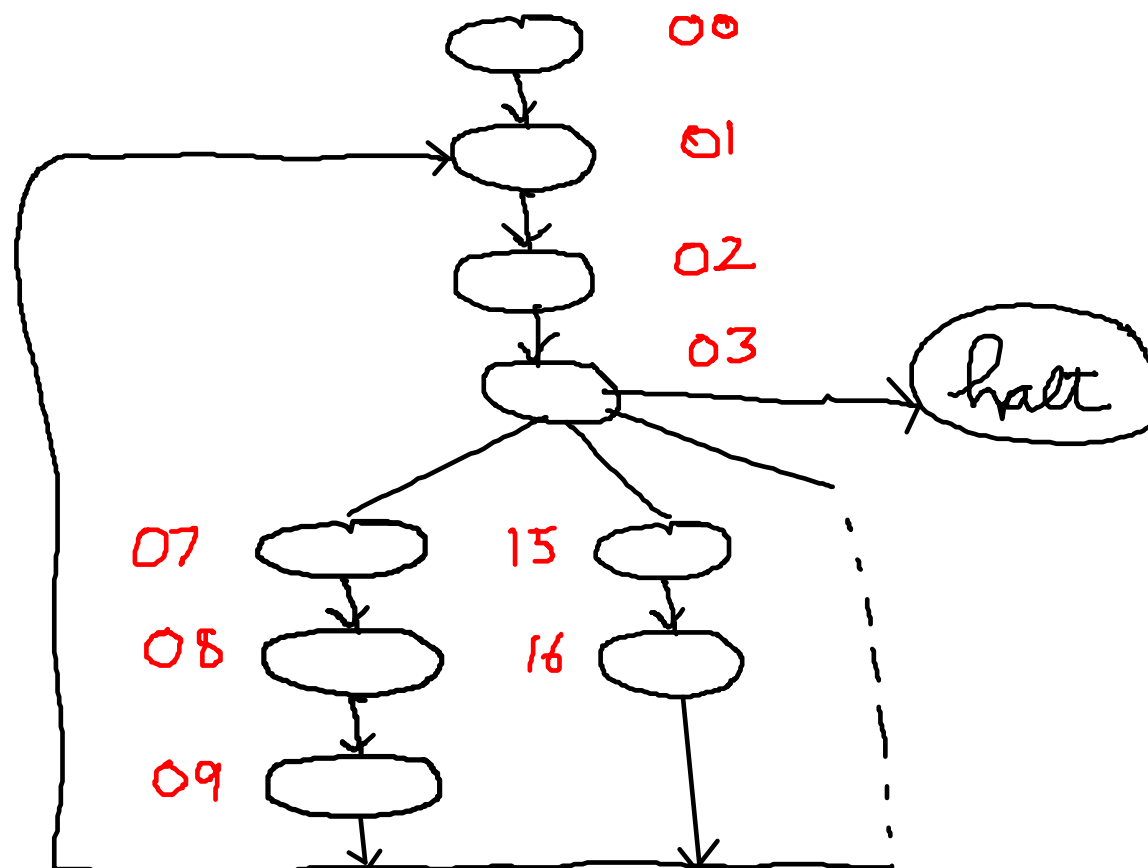


FSM Implementation Example

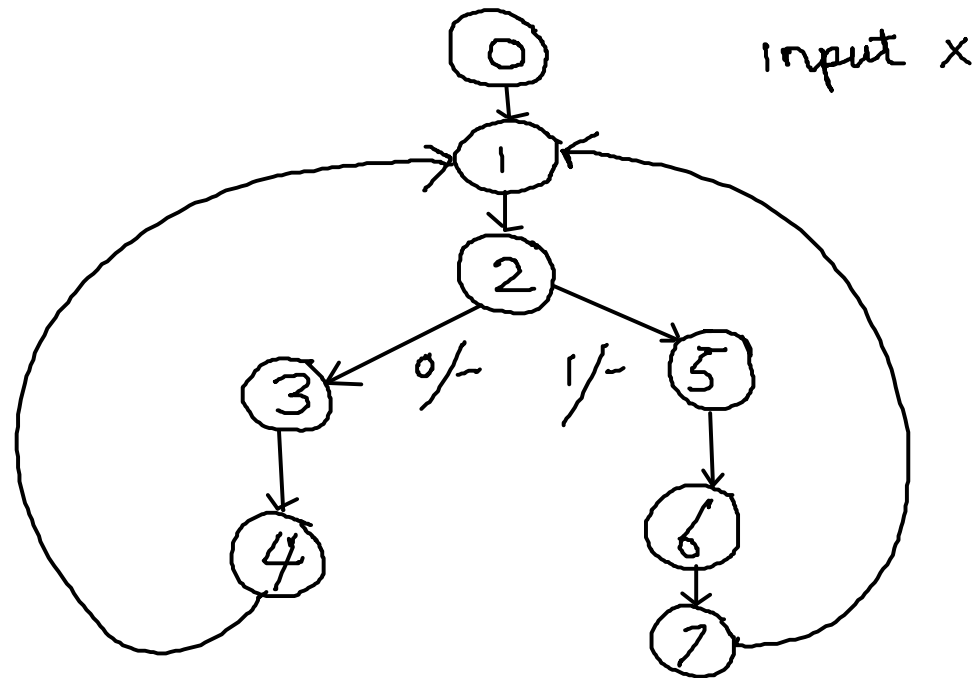- implement state transition using a 3-bit counter



FSM Implementation Example cont.

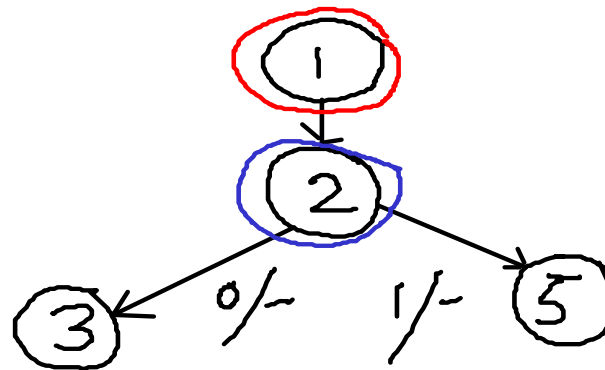

Q

Q2	Q1	Q0	X	LD	CE	SCLR	L2	L1	L0
0	0	1	0	0	1	0	-	-	-
0	0	1	1	0	1	0	-	-	-
0	1	0	0	0	1	0	-	-	-
0	1	0	1	1	-	-	1	0	1

FSM Implementation Example cont.

Q2	Q1	Q0	X	LD	CE	SCLR	L2	L1	L0	<u>State</u>
0	0	0	0	0	1	0	-	-	-	0
0	0	0	1	0	1	0	-	-	-	1
0	0	1	0	0	1	0	-	-	-	2
0	0	1	1	0	1	0	-	-	-	3
0	1	0	0	0	1	0	-	-	-	4
0	1	0	1	1	-	-	1	0	1	5
0	1	1	0	0	1	0	-	-	-	6
0	1	1	1	0	1	0	-	-	-	7
1	0	0	0	1	-	-	0	0	1	
1	0	0	1	1	-	-	0	0	1	
1	0	1	0	0	1	0	-	-	-	
1	0	1	1	0	1	0	-	-	-	
1	1	0	0	0	1	0	-	-	-	
1	1	0	1	0	1	0	-	-	-	
1	1	1	0	1	-	-	0	0	1	
1	1	1	1	1	-	-	0	0	1	

State Minimization

- Equivalent States
 - two states are equivalent if they have the same next state and output
- Minimization Techniques
 - Row Comparison
 - Implication Table

Row Comparison)


Current State	Next State		Output
	X=0	X=1	
S0	S1	S0	0
S1	S2	S0	0
S2	S3	S6	0
S3	S0	S4	0
S4	S5	S0	0
S5	S0	S0	1
S6	S7	S0	0
S7	S8	S0	0
S8	S0	S0	1

Replace S8 with S5

Replace S7 with S4

Implication Table

- contrived example

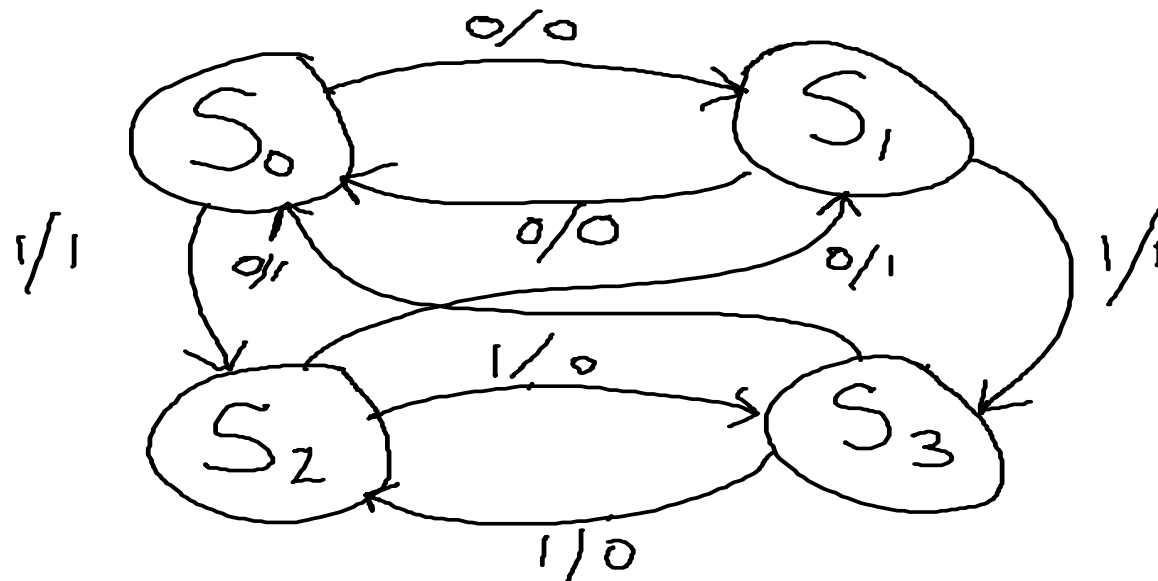


Implication Table cont.

Current State	Next State		Output	
	X=0	X=1	X=0	X=1
S0	S1	S2	0	1
S1	S0	S3	0	1
S2	S1	S3	1	0
S3	S0	S2	1	0

S1	2=3		
S2	X	X	
S3	X	X	0=1
	S0	S1	S2


S2 ≡ S3
S0 ≡ S1

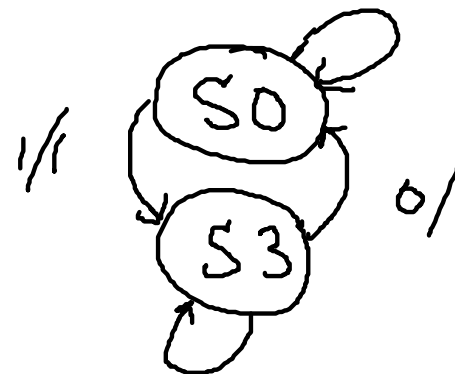

Implication Table

- a second example

Current State	Next State		Output
	X=0	X=1	
S0	S1	S3	0
S1	S2	S4	0
S2	S0	S3	0
S3	S4	S5	1
S4	S3	S6	1
S5	S7	S6	1
S6	S7	S5	1
S7	S5	S7	0

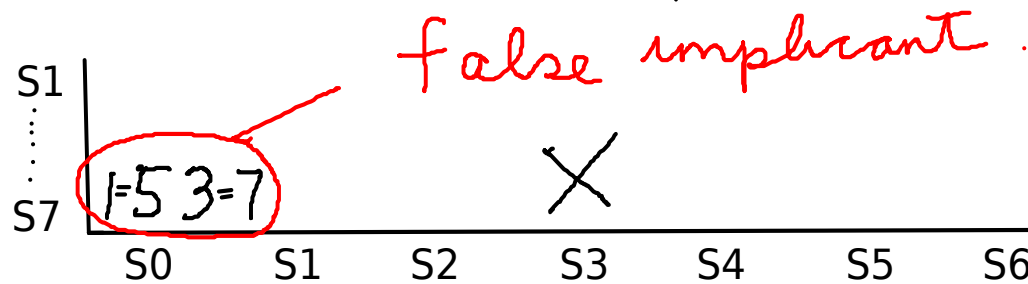

Implication Table cont.

S1	$1=2$ $3=4$						
S2	$0=1$	$0=2$ $3=4$					
S3	X	X	X				
S4	X	X	X	$3=4$ $5=6$			
S5	X	X	X	$4=7$ $5=6$	$3=7$		
S6	X	X	X	$4=7$	$6=7$ $3=7$	$5=6$	
S7	$1=5$ $3=7$	$2=5$ $4=7$	$0=5$ $3=7$	X	X	X	X
	S0	S1	S2	S3	S4	S5	S6

Implication Table cont.

S1	$1=2$ $3=4$						
S2	$0=1$	$0=2$ $3=4$					
S3	X	X	X				
S4	X	X	X	$3=4$ $5=6$			
S5	X	X	X	$4=7$ $5=6$	$3=7$		
S6	X	X	X	$4=7$	$6=7$ $3=7$	$5=6$	
S7	$1=5$ $3=7$	$2=5$ $4=7$	$0=5$ $3=7$	X	X	X	X
	S0	S1	S2	S3	S4	S5	S6

$S0 \equiv S1 \equiv S2$

$S3 \equiv S4$

$S5 \equiv S6$